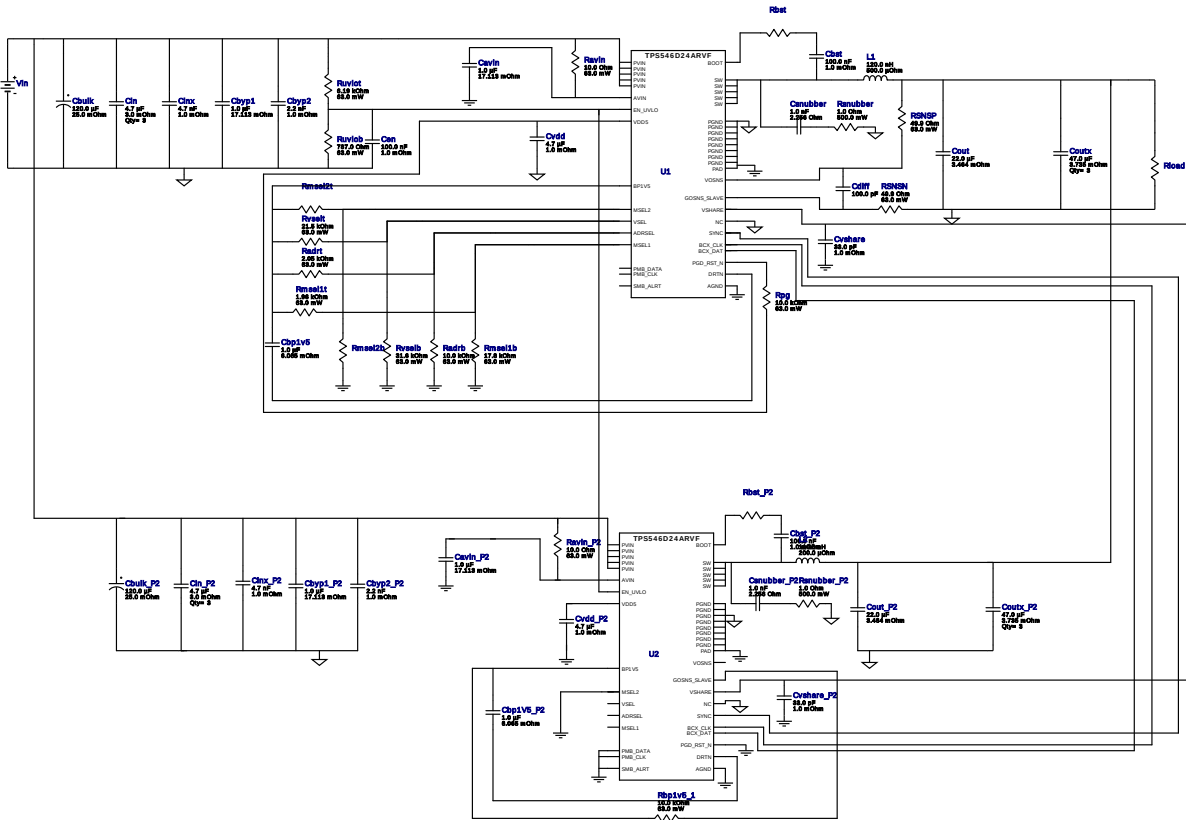


WEBENCH® Design Report

Design : 94 TPS546D24ARVFR
TPS546D24ARVFR 12V to 2.8V @ 60A - BitaxeBonanza

VinMin = 11.0V
VinMax = 13.0V
Vout = 2.8V
Vout Sch = 2.8V
Iout = 60.0A

Device = TPS546D24ARVFR
Topology = Buck
Created = 2024-04-25 15:33:45.860
BOM Cost = \$19.06
BOM Count = 63
Total Pd = 17.77W



1. Do not place Rmsel2b, Rmsel2t resistors. Place 0 Ohm resistor for Rbst.

Design Alerts

TPS546D24A Design

The TPS546D24A is a PMBus(TM) device with key features listed below: PMBus(TM) features marked with * are included in WEBENCH(R) Power Designer. - Adaptive Voltage Scaling (AVS) through VOUT_COMMAND*, - Output voltage and current monitoring, - Thermal Shutdown, - Programmable over current protection, - OCP,OV, UV, OT Levels, - Selectable Internal Compensation*, - Selectable Switching Frequency*, - Turn-On and Turn-Off Delays, - UVLO*, Soft-Start*,OCP* and Soft-Stop. Use the Advanced Options on the left side to set the PMBus(TM) commands. Please refer to the TPS546D24A datasheet and visit <http://www.ti.com/pmbus> for more information.

Electrical BOM





Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cavin	MuRata	GRM188R61E105KA12D Series= X5R	Cap= 1.0 uF ESR= 17.113 mOhm VDC= 25.0 V IRMS= 979.39 mA	1	\$0.02	0603 5 mm ²
Cavin_P2	MuRata	GRM188R61E105KA12D Series= X5R	Cap= 1.0 uF ESR= 17.113 mOhm VDC= 25.0 V IRMS= 979.39 mA	1	\$0.02	0603 5 mm ²
Cbp1V5_P2	MuRata	GRM188R60J105KA01D Series= X5R	Cap= 1.0 uF ESR= 6.065 mOhm VDC= 6.3 V IRMS= 1.36934 A	1	\$0.01	0603 5 mm ²







Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cbp1v5	MuRata	GRM188R60J105KA01D Series= X5R	Cap= 1.0 uF ESR= 6.065 mOhm VDC= 6.3 V IRMS= 1.36934 A	1	\$0.01	 0603 5 mm²
Cbst	MuRata	GRM155R71C104KA88D Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm²
Cbst_P2	MuRata	GRM155R71C104KA88D Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm²
Cbulk	Panasonic	20SVPF120M Series= SVPF	Cap= 120.0 uF ESR= 25.0 mOhm VDC= 20.0 V IRMS= 3.2 A	1	\$0.57	 CAPSMT_62_F61 74 mm²
Cbulk_P2	Panasonic	20SVPF120M Series= SVPF	Cap= 120.0 uF ESR= 25.0 mOhm VDC= 20.0 V IRMS= 3.2 A	1	\$0.57	 CAPSMT_62_F61 74 mm²
Cbyp1	MuRata	GRM188R61E105KA12D Series= X5R	Cap= 1.0 uF ESR= 17.113 mOhm VDC= 25.0 V IRMS= 979.39 mA	1	\$0.02	 0603 5 mm²
Cbyp1_P2	MuRata	GRM188R61E105KA12D Series= X5R	Cap= 1.0 uF ESR= 17.113 mOhm VDC= 25.0 V IRMS= 979.39 mA	1	\$0.02	 0603 5 mm²
Cbyp2	MuRata	GRM155R61E222KA01D Series= X5R	Cap= 2.2 nF ESR= 1.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm²
Cbyp2_P2	MuRata	GRM155R61E222KA01D Series= X5R	Cap= 2.2 nF ESR= 1.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm²
Cdiff	Kemet	C0201C101K3GACTU Series= C0G/NP0	Cap= 100.0 pF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm²
Cen	MuRata	GRM155R71A104KA01D Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm²
Cin	MuRata	GRM31CR71H475KA12L Series= X7R	Cap= 4.7 uF ESR= 3.0 mOhm VDC= 50.0 V IRMS= 4.98 A	3	\$0.10	 1206 11 mm²
Cin_P2	MuRata	GRM31CR71H475KA12L Series= X7R	Cap= 4.7 uF ESR= 3.0 mOhm VDC= 50.0 V IRMS= 4.98 A	3	\$0.10	 1206 11 mm²
Cinx	MuRata	GRM155R71E472KA01D Series= X7R	Cap= 4.7 nF ESR= 1.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm²
Cinx_P2	MuRata	GRM155R71E472KA01D Series= X7R	Cap= 4.7 nF ESR= 1.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm²
Cout	Taiyo Yuden	MSASJ21GBC6226MTNA01 Series= X6S	Cap= 22.0 uF ESR= 3.464 mOhm VDC= 6.3 V IRMS= 3.7578 A	1	\$0.07	 0805 7 mm²







Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cout_P2	Taiyo Yuden	MSASJ21GBC6226MTNA01 Series= X6S	Cap= 22.0 uF ESR= 3.464 mOhm VDC= 6.3 V IRMS= 3.7578 A	1	\$0.07	 0805 7 mm ²
Coutx	MuRata	GRM31CR60J476KE19L Series= X5R	Cap= 47.0 uF ESR= 3.735 mOhm VDC= 6.3 V IRMS= 4.091 A	3	\$0.13	 1206_190 11 mm ²
Coutx_P2	MuRata	GRM31CR60J476KE19L Series= X5R	Cap= 47.0 uF ESR= 3.735 mOhm VDC= 6.3 V IRMS= 4.091 A	3	\$0.13	 1206_190 11 mm ²
Csubber	TDK	CGA2B2X7R1H102K050BA Series= X7R	Cap= 1.0 nF ESR= 2.25564 Ohm VDC= 50.0 V IRMS= 280.466 mA	1	\$0.01	 0402 3 mm ²
Csubber_P2	TDK	CGA2B2X7R1H102K050BA Series= X7R	Cap= 1.0 nF ESR= 2.25564 Ohm VDC= 50.0 V IRMS= 280.466 mA	1	\$0.01	 0402 3 mm ²
Cvdd	MuRata	GRM155R61A475MEAAD Series= X5R	Cap= 4.7 uF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.02	 0402_065 3 mm ²
Cvdd_P2	MuRata	GRM155R61A475MEAAD Series= X5R	Cap= 4.7 uF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.02	 0402_065 3 mm ²
Cvshare	MuRata	GRM1555C1E330JA01D Series= C0G/NP0	Cap= 33.0 pF ESR= 1.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
Cvshare_P2	MuRata	GRM1555C1E330JA01D Series= C0G/NP0	Cap= 33.0 pF ESR= 1.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
L1	Coiltronics	FP0807R1-R12-R	L= 120.0 nH 500.0 µOhm	1	\$1.22	 FP0807 89 mm ²
L2	Coilcraft	SLC1480-111MLB	L= 110.0 nH 200.0 µOhm	1	\$0.78	 SLC1480 231 mm ²
L2	Coilcraft	SLC1480-111MLB	L= 110.0 nH 200.0 µOhm	1	\$0.78	 SLC1480 231 mm ²
L2	Coilcraft	SLC1480-111MLB	L= 110.0 nH 200.0 µOhm	1	\$0.78	 SLC1480 231 mm ²







Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
L2	Coilcraft	SLC1480-111MLB	L= 110.0 nH 200.0 µOhm	1	\$0.78	 SLC1480 231 mm ²
L2	Coilcraft	SLC1480-111MLB	L= 110.0 nH 200.0 µOhm	1	\$0.78	 SLC1480 231 mm ²
L2	Coilcraft	SLC1480-111MLB	L= 110.0 nH 200.0 µOhm	1	\$0.78	 SLC1480 231 mm ²
L2	Coilcraft	SLC1480-111MLB	L= 110.0 nH 200.0 µOhm	1	\$0.78	 SLC1480 231 mm ²
L2	Coilcraft	SLC1480-111MLB	L= 110.0 nH 200.0 µOhm	1	\$0.78	 SLC1480 231 mm ²
RSNSN	Vishay-Dale	CRCW040249R9FKED Series= CRCW..e3	Res= 49.9 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
RSNSP	Vishay-Dale	CRCW040249R9FKED Series= CRCW..e3	Res= 49.9 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Radrb	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Radrt	Vishay-Dale	CRCW04022K05FKED Series= CRCW..e3	Res= 2.05 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Ravin	Vishay-Dale	CRCW040210R0FKED Series= CRCW..e3	Res= 10.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Ravin_P2	Vishay-Dale	CRCW040210R0FKED Series= CRCW..e3	Res= 10.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rbp1v5_1	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rmsel1b	Vishay-Dale	CRCW040217K8FKED Series= CRCW..e3	Res= 17.8 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rmsel1t	Vishay-Dale	CRCW04021K96FKED Series= CRCW..e3	Res= 1.96 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
Rpg	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Rsnubber	Stackpole Electronics Inc	CSR1206FT1R00 Series= ?	Res= 1.0 Ohm Power= 500.0 mW Tolerance= 1.0%	1	\$0.04	 1206 11 mm²
Rsnubber_P5	Stackpole Electronics Inc	CSR1206FT1R00 Series= ?	Res= 1.0 Ohm Power= 500.0 mW Tolerance= 1.0%	1	\$0.04	 1206 11 mm²
Ruvlob	Vishay-Dale	CRCW0402787RFKED Series= CRCW..e3	Res= 787.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
Ruvlot	Vishay-Dale	CRCW04026K19FKED Series= CRCW..e3	Res= 6.19 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
Rvselb	Vishay-Dale	CRCW040231K6FKED Series= CRCW..e3	Res= 31.6 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
Rvselt	Vishay-Dale	CRCW040221K5FKED Series= CRCW..e3	Res= 21.5 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
U1	Texas Instruments	TPS546D24ARVFR	Switcher	1	\$4.22	 RVF0040A 63 mm²
U2	Texas Instruments	TPS546D24ARVFR	Switcher	1	\$4.22	LQFN-CLIP 0 mm²

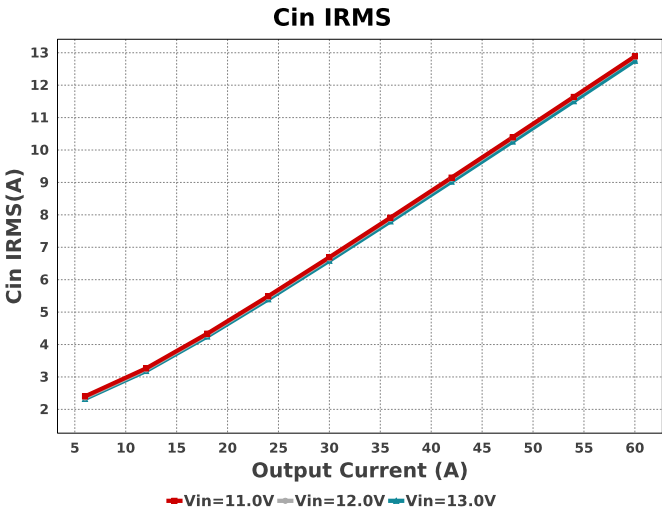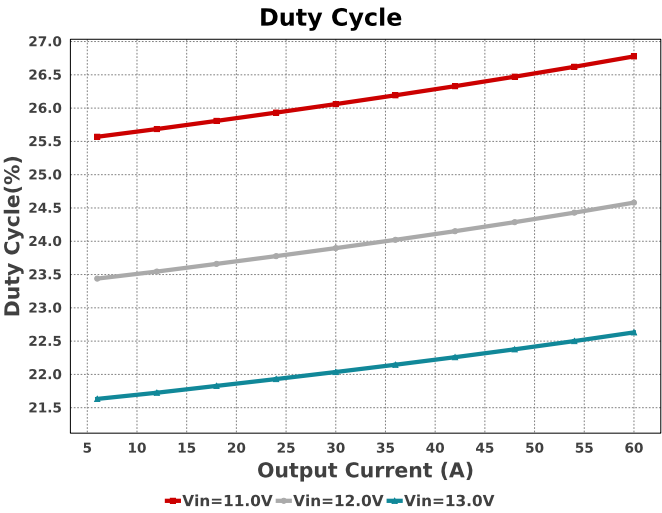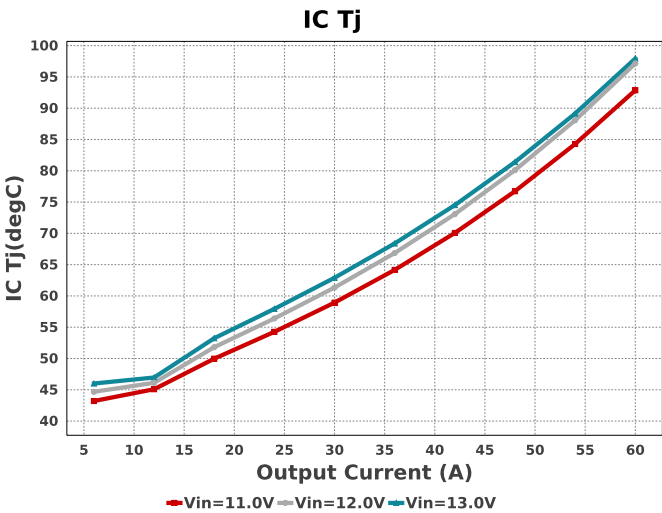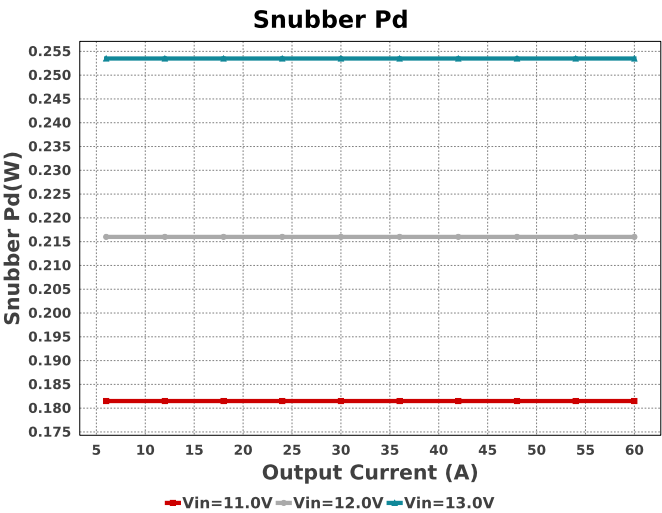

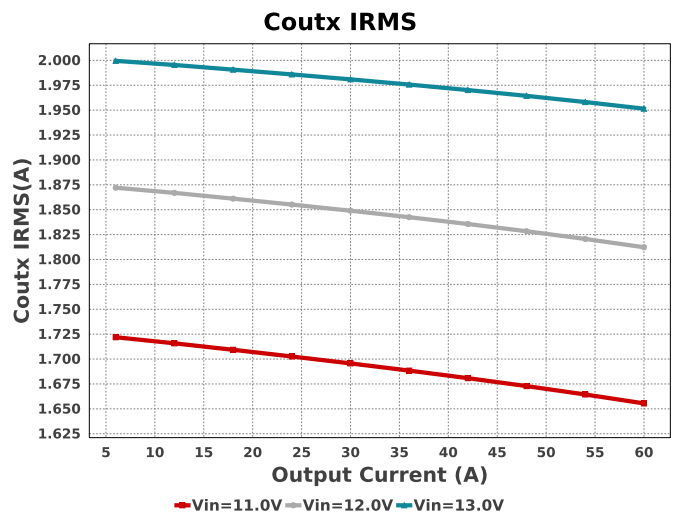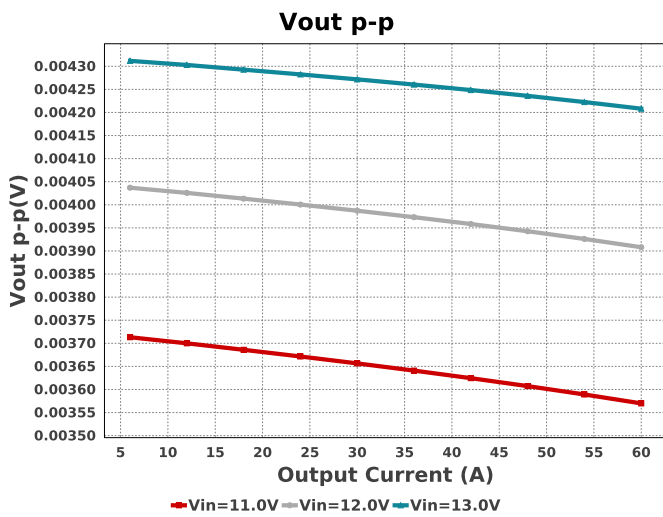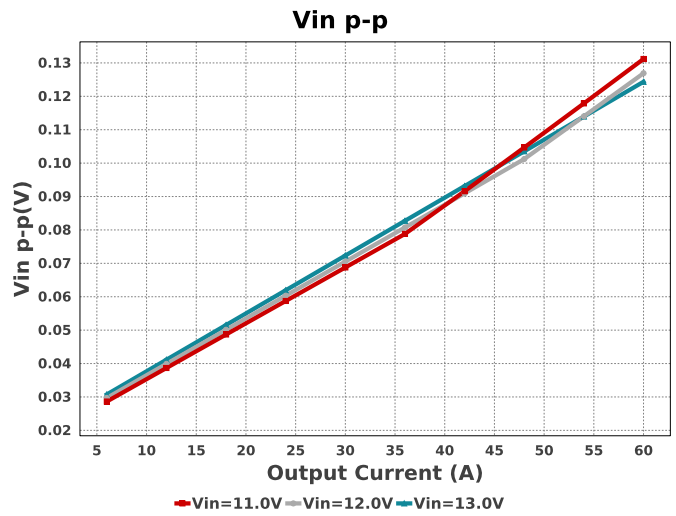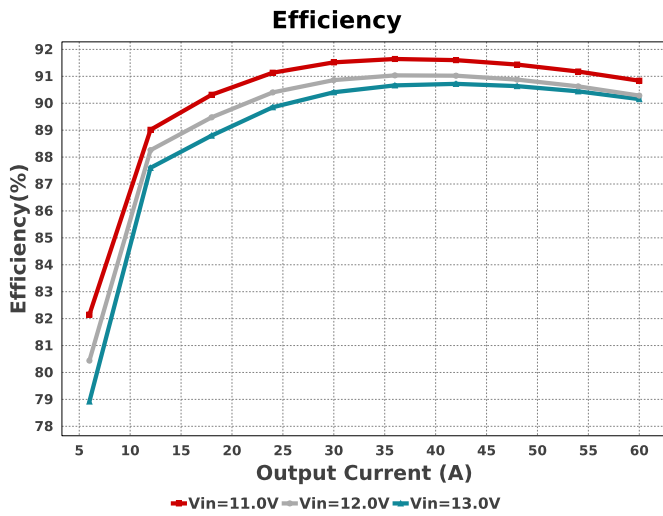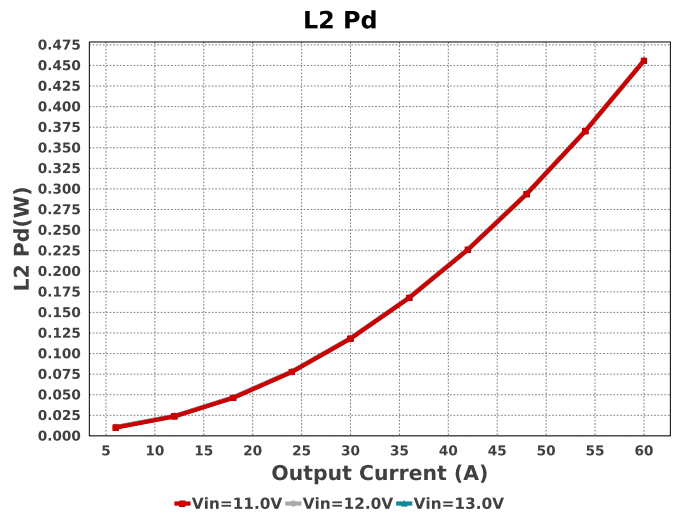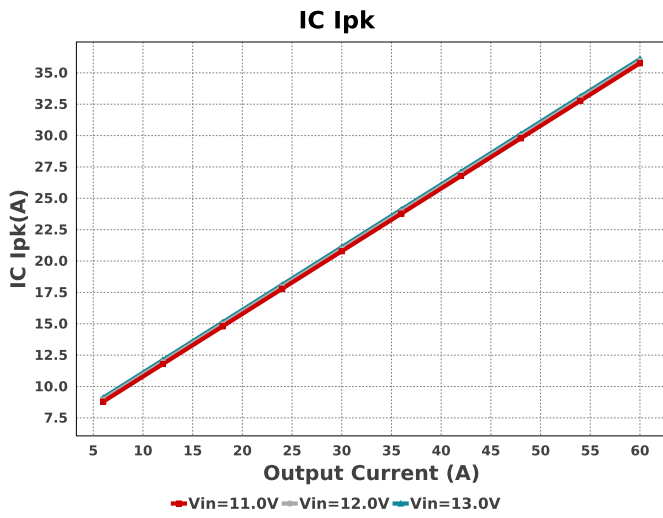

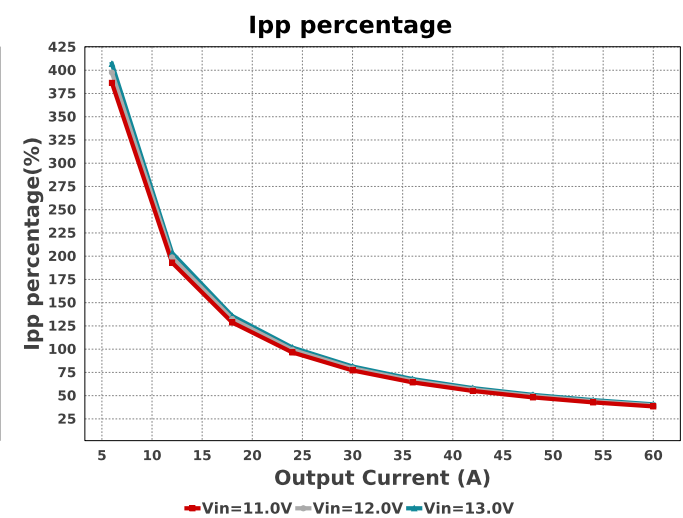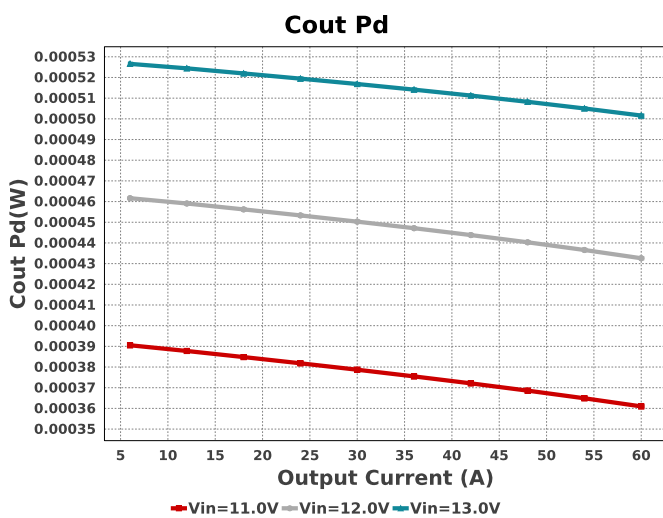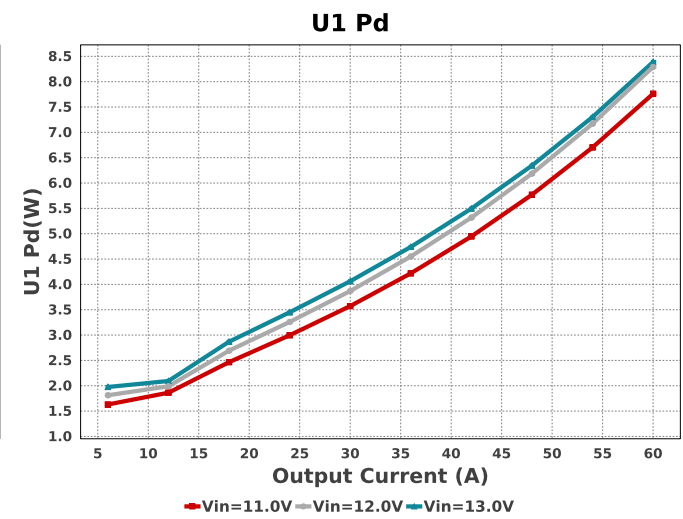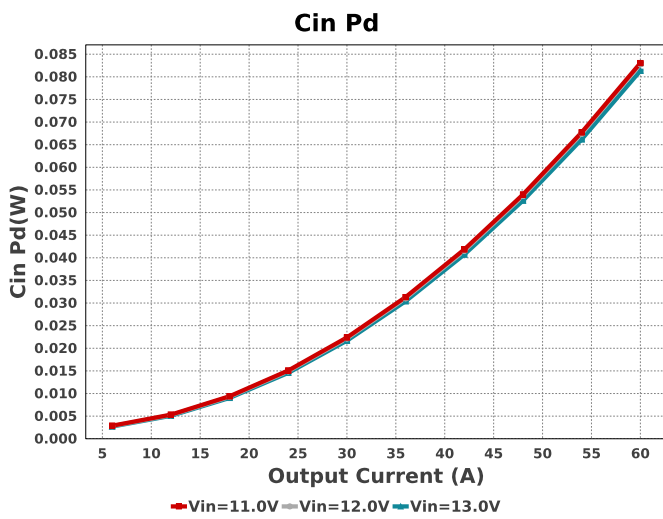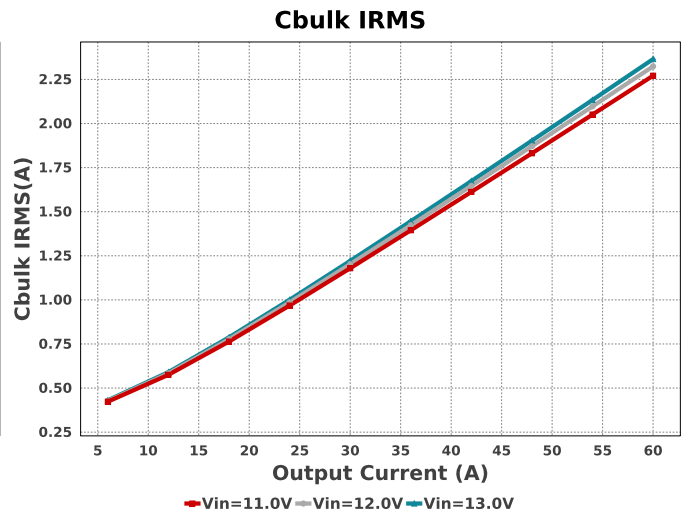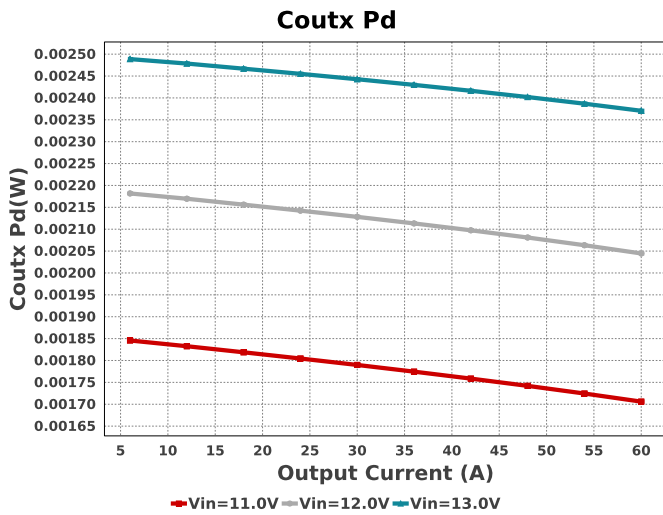

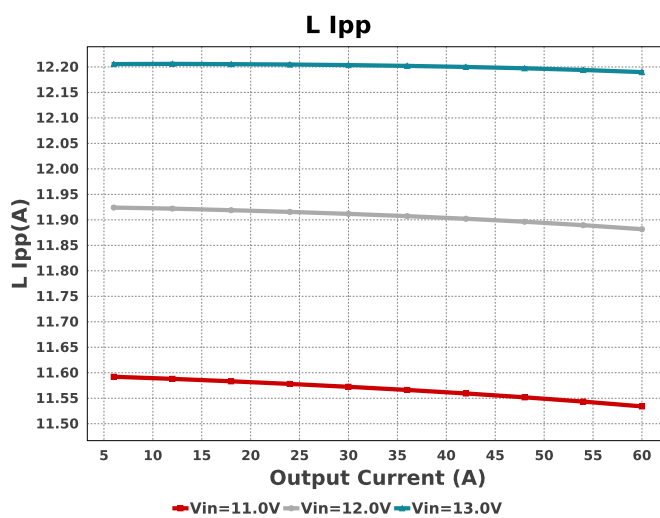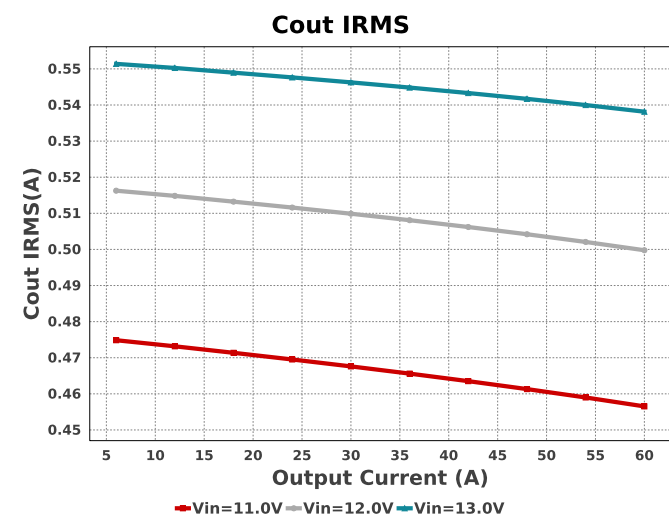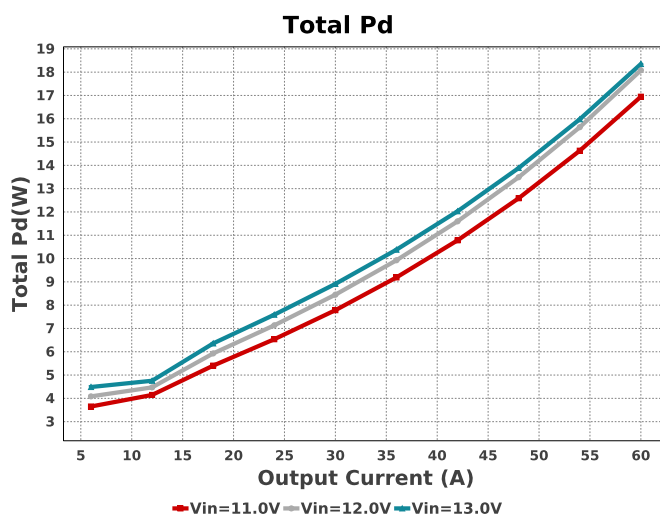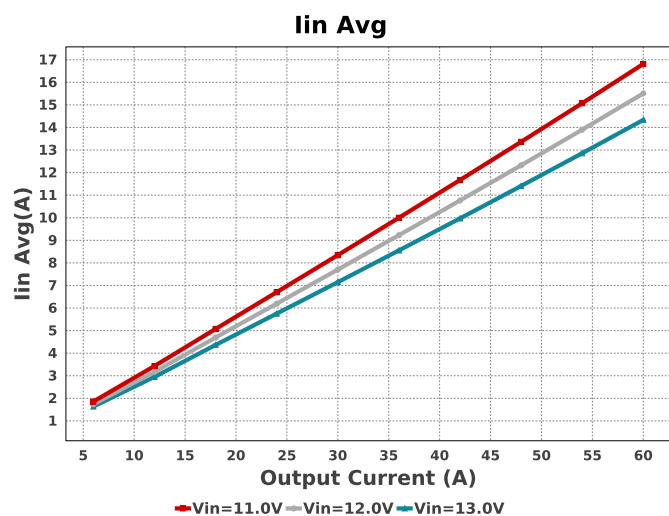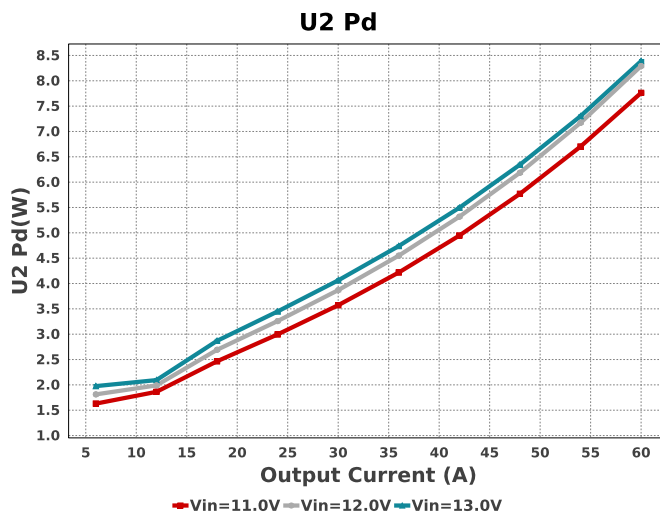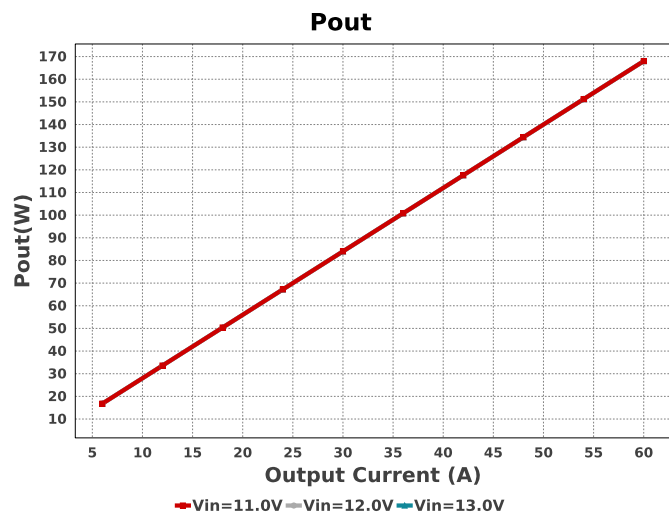

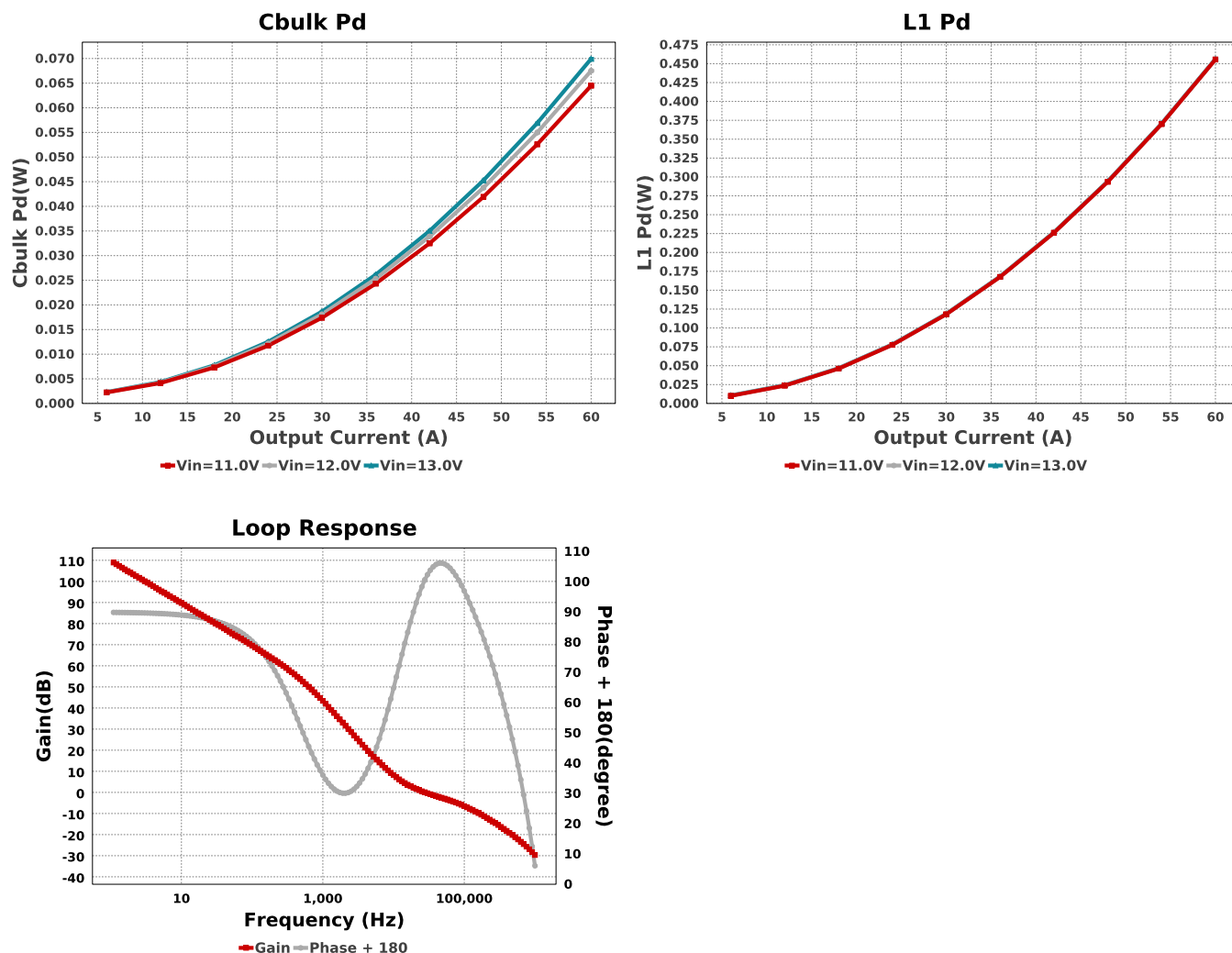

Operating Values

#	Name	Value	Category	Description
1.	Cbulk IRMS	2.37 A	Capacitor	Bulk capacitor RMS ripple current
2.	Cbulk Pd	70.202 mW	Capacitor	Bulk capacitor power dissipation
3.	Cin IRMS	12.779 A	Capacitor	Input capacitor RMS ripple current
4.	Cin Pd	81.645 mW	Capacitor	Input capacitor power dissipation
5.	Cout IRMS	586.752 mA	Capacitor	Output capacitor RMS ripple current
6.	Cout Pd	596.29 μ W	Capacitor	Output capacitor power dissipation
7.	Coutx IRMS	2.128 A	Capacitor	Output capacitor_x RMS ripple current
8.	Coutx Pd	2.818 mW	Capacitor	Output capacitor_x power loss
9.	Fpi	1.658 MHz	Compensation	Current Loop Pole Frequency
10.	Fpv	636.62 kHz	Compensation	Voltage Loop Pole Frequency
11.	Fzi	49.741 kHz	Compensation	Current Loop Zero Frequency
12.	Fzv	15.915 kHz	Compensation	Voltage Loop Zero Frequency
13.	ILOOP Gain	6.501	Compensation	Recommended Current Loop Mid-band Gain
14.	VLOOP Gain	4.391	Compensation	Recommended Voltage Loop Mid-band Gain
15.	Zout (Fco)	23.804 mOhm	Compensation	Output Impedance at Crossover Frequency
16.	Zout (Fsw)	711.598 μ Ohm	Compensation	Output Impedance at Switching Frequency
17.	IC Ipk	36.634 A	IC	Peak switch current in IC
18.	IC Tj	97.798 degC	IC	IC junction temperature
19.	ICThetaJA Effective	8.1 degC/W	IC	Effective IC Junction-to-Ambient Thermal Resistance
20.	Iin Avg	14.29 A	IC	Average input current
21.	U1 Pd	8.37 W	IC	IC power dissipation
22.	U2 Pd	8.37 W	IC	IC power dissipation
23.	Ipp percentage	44.227 %	Inductor	Inductor ripple current percentage (with respect to average inductor current)
24.	L Ipp	13.268 A	Inductor	Peak-to-peak inductor ripple current
25.	L1 Pd	182.93 mW	Inductor	Inductor power dissipation
26.	L2 Pd	182.93 mW	Inductor	Inductor power dissipation
27.	CPI	3.2 pF	PMBus	Selectable compensation parameter through pinstrapping
28.	CPV	6.25 pF	PMBus	Selectable compensation parameter through pinstrapping
29.	CZI	106.656 pF	PMBus	Selectable compensation parameter through pinstrapping
30.	CZV	250.0 pF	PMBus	Selectable compensation parameter through pinstrapping
31.	GMI	200.0 μ S	PMBus	Selectable compensation parameter through pinstrapping

#	Name	Value	Category	Description
32.	GMV	50.0 μ S	PMBus	Selectable compensation parameter through pinstrapping
33.	PMBus Vout Command	2.8	PMBus	PMBus Vout Command
34.	PMBus Vout Scale Loop	125.0 m	PMBus	PMBus Vout Scale Loop
35.	RV1	30.0 kOhm	PMBus	Selectable compensation parameter through pinstrapping
36.	RVV	40.0 kOhm	PMBus	Selectable compensation parameter through pinstrapping
37.	Cbulk Pd	70.202 mW	Power	Bulk capacitor power dissipation
38.	Cin Pd	81.645 mW	Power	Input capacitor power dissipation
39.	Cout Pd	596.29 μ W	Power	Output capacitor power dissipation
40.	Coutx Pd	2.818 mW	Power	Output capacitor _x power loss
41.	L1 Pd	182.93 mW	Power	Inductor power dissipation
42.	L2 Pd	182.93 mW	Power	Inductor power dissipation
43.	Snubber Pd	253.5 mW	Power	Snubber Power Dissipation
44.	Total Pd	17.769 W	Power	Total Power Dissipation
45.	U1 Pd	8.37 W	Power	IC power dissipation
46.	U2 Pd	8.37 W	Power	IC power dissipation
47.	BOM Count	63	System Information	Total Design BOM count
48.	Cross Freq	32.463 kHz	System Information	Bode plot crossover frequency
49.	Duty Cycle	22.559 %	System Information	Duty cycle
50.	Efficiency	90.435 %	System Information	Steady state efficiency
51.	FootPrint	2.432 k mm ²	System Information	Total Foot Print Area of BOM components
52.	Frequency	1.5 MHz	System Information	Switching frequency
53.	Gain Marg	-30.24 dB	System Information	Bode Plot Gain Margin
54.	Iout	60.0 A	System Information	Iout operating point
55.	Low Freq Gain	109.688 dB	System Information	Gain at 1Hz
56.	Mode	CCM	System Information	Conduction Mode
57.	Phase Marg	103.55 deg	System Information	Bode Plot Phase Margin
58.	Pout	168.0 W	System Information	Total output power
59.	Total BOM	\$19.06	System Information	Total BOM Cost
60.	Vin	13.0 V	System Information	Vin operating point
61.	Vin p-p	126.143 mV	System Information	Peak-to-peak input voltage
62.	Vout	2.8 V	System Information	Operational Output Voltage
63.	Vout Tolerance	285.71 m%	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
64.	Vout p-p	4.588 mV	System Information	Peak-to-peak output ripple voltage

Design Inputs

	Name	Value	Description
	Iout	60.0	Maximum Output Current
	VinMax	13.0	Maximum input voltage
	VinMin	11.0	Minimum input voltage
	Vout	2.8	Output Voltage
	base_pn	TPS546D24A	Base Product Number
	source	DC	Input Source Type
	Ta	30.0	Ambient temperature
1.	Vout Sch	2.8	Output voltage selected

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 11.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

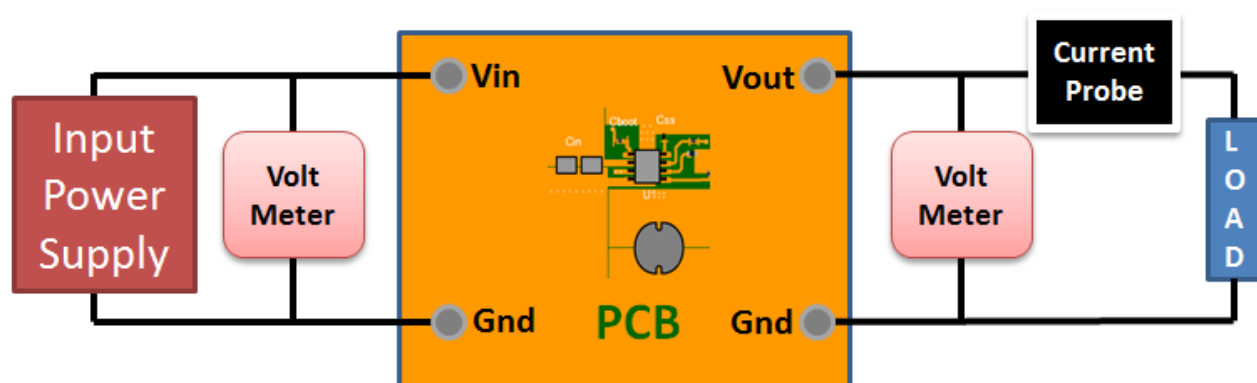

Design Assistance

1. Master key : 4403CD56E2ECE12A[v1]
2. **TPS546D24A** Product Folder : <http://www.ti.com/product/TPS546D24A> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.